$$G_1 = G_2 = 0.2$$
S,  $G_3 = 0.1$ S. The matrix equation is  $\begin{bmatrix} 0.2 + 0.2 & -0.2 \\ -0.2 & 0.2 + 0.1 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 1 \\ -0.5 \end{bmatrix}$  or  $\begin{bmatrix} 0.4 & -0.2 \\ -0.2 & 0.3 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 1 \\ -0.25 \end{bmatrix}$ . The easiest way in practice is to use a computer to solve this matrix equation. Using R we will code it as

```
G=matrix(c(0.4,-0.2,-0.2,0.3),ncol=2,byrow=TRUE)
Is=c(1,-0.25)
Vn <- solve(G,Is)
```

Note the matrix, current, and voltage vectors are


Observe that the current sources can be thought of current *injection* at node 1 and current *export* (or negative injection) at node 2. These values have forced the voltages  $V_1$  and  $V_2$  to acquire the values shown. We can think of power injection at node 1  $P_1 = V_1 I_{s_1}$  and power injection (negative or export) at node 2  $P_2 = V_2 I_{s_2}$ . This terminology becomes useful later when we talk about power flow in the grid.

## Example 3.9

Calculate power injected at node 1 as  $P_1 = V_1I_{s1} = 3.125 \times 1 = 3.125$  W and power injected (negative or exported) at node 2 as  $P_2 = V_2I_{s2} = 1.25 \times (-0.25) = -0.3125$  W. The difference of 2.8125 W must be the power dissipated in the circuit. If we calculate the sum of power dissipated in all three resistors, we get  $P_{diss} = V_1^2 G_1 + V_2^2 G_3 + (V_2 - V_1)^2 G_2 = 2.8125$  W.

## 3.3.4 MESH ANALYSIS

Mesh analysis is the dual of nodal analysis when applied to independent loops (i.e., meshes). Think of the circuit in Figure 3.12 and setting up a system of equations for the unknown currents using KVL

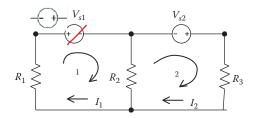

**FIGURE 3.12** A simple circuit to explain mesh analysis.

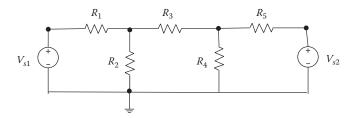


FIGURE 3.24 Circuit to solve by mesh analysis.

What is the power lost in the wires and power delivered to the bulbs? Discuss the results. How could you reduce wire power loss?

3.8. Based on Problem 2.11 from Masters [5], in a home, lights draw 20 A and are on 10 hr every day, and are located about 30 m from the wiring panel. You know that 12-gauge wire can carry this current but you are considering whether to buy 10-gauge wire to save money as potential lower wire loss Assume "Romex" wire (2 wire + ground) costs \$1.50 per m for 12 gauge and \$2.00 per ft for 10 gauge, and utility rates are \$0.10 per kWh. How many years (simple payback period) would it take to pay the extra cost of heavier duty wire?

## **REFERENCES**

- 1. Irwin, J.D., and R.M. Nelms, Basic Engineering Circuit Analysis. 11th edition. 2011: Wiley. 688 pp.
- 2. Hayt, W., J. Kemmerly, and S. Durbin, *Engineering Circuit Analysis*. Eighth edition. 2012: McGraw Hill. 880 pp.
- 3. Alexander, C.K., and M.N.O. Sadiku, *Fundamentals of Electric Circuits*. Third edition. 2007: McGraw Hill. 1056 pp.
- 4. Hemami, A., *Electricity and Electronics for Renewable Energy Technology: An Introduction.* Power Electronics and Applications Series, M.H. Rashid. 2016, Boca Raton, Florida: CRC Press/Taylor & Francis. 796 pp.
- 5. Masters, G.M., *Renewable and Efficient Electric Power Systems*. Second edition. 2013: Wiley-IEEE Press. 690 pp.